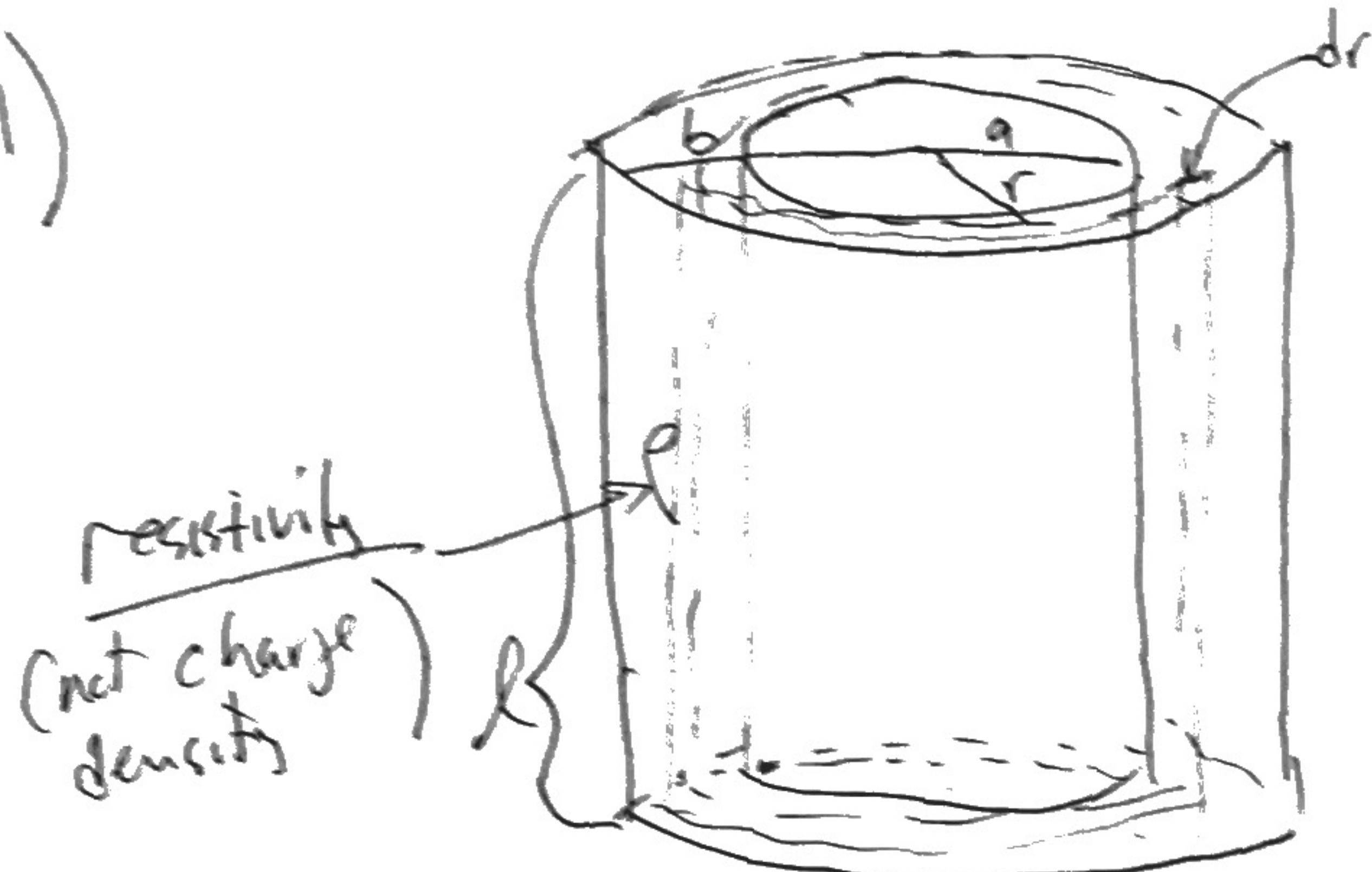


Problem Set #4 Solutions

1

1)



Note: we want resistance ~~that~~ between inner and outer cylinders, not along the length of the cylinders.

$$\text{In general: } R = \rho \frac{\text{length}}{A} \quad (\text{eq 4.17})$$

~~length~~  
in PM  
~~A~~ cross sectional area

~~Here,  $\cancel{dR = l \cdot 2\pi r}$ , so this is the length between the two ends.~~

~~However,~~  $A = \text{cross-sectional area of a thin cylindrical shell at radius } r \Rightarrow l \cdot 2\pi r$ .

Now, we can view this resistor as a collection of series resistors, one from each cylindrical shell of radius  $r$ . In other words,

$R_{\text{TOT}} = \int_{r=0}^{r=b} dR$  where  $dR$  is the small amount of resistance coming from the shell at radius  $r$ . The length of this small resistor (shell) is  $dr$ , so that the resistance of one shell is given by  $dR$ .

$dR = \rho \frac{L}{A} = \rho \frac{dr}{l \cdot 2\pi r}$ . Thus we have, summing over all the little shells,


$$R_{\text{TOT}} = \int_{r=0}^{r=b} \frac{\rho dr}{2\pi r l} = \frac{\rho}{2\pi l} \ln(b/a).$$

units ✓

Note: makes sense in limits  $l \rightarrow \infty$  ( $R \rightarrow 0$ ) and  $b \rightarrow a$  ( $R \rightarrow 0$ ).

(2)
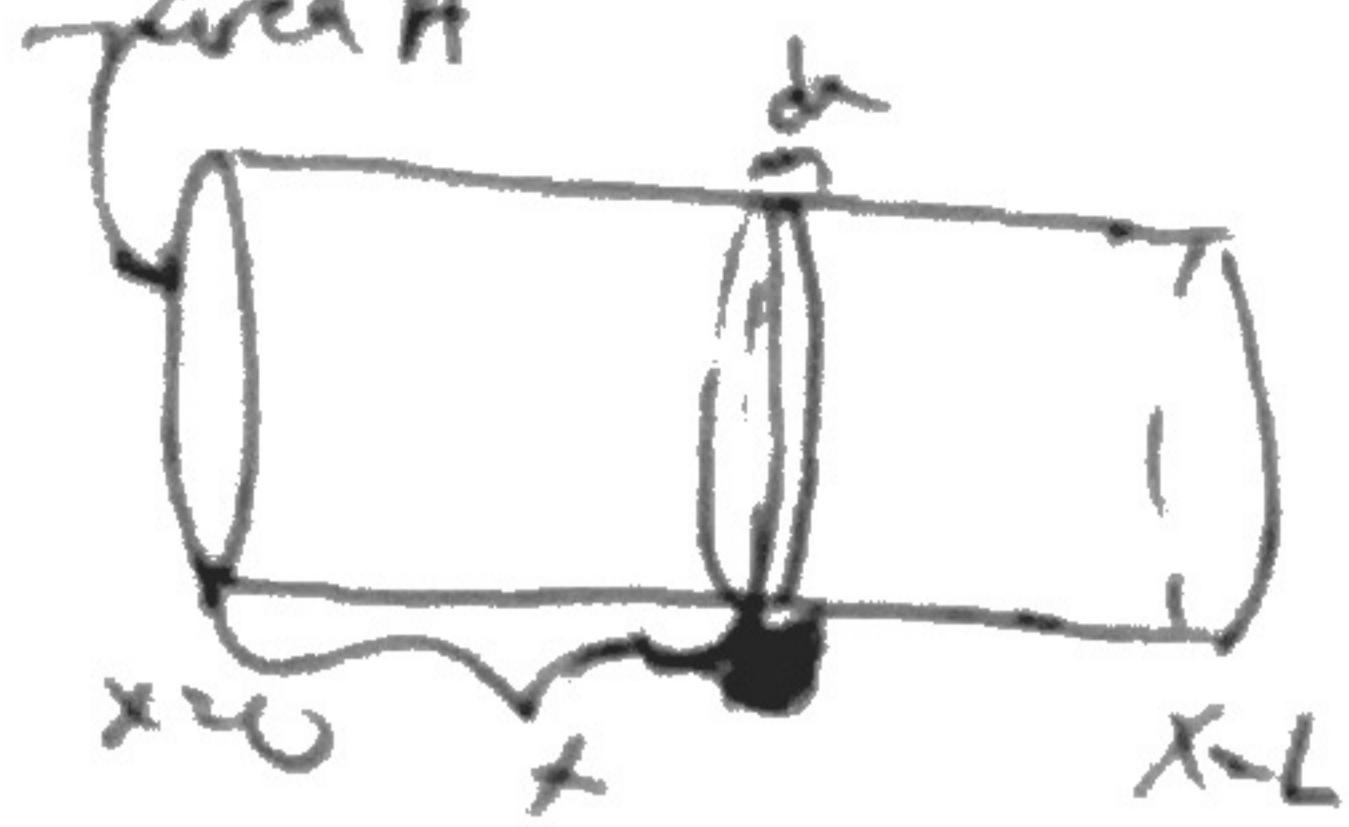
#2] Again we can (and should) think of this rod as a bunch of thin



resistors, each located at  $0 \leq x \leq L$   
with thickness  $dx$  and resistance  $dR$

given by  $dR = \rho(x) \frac{dx}{A}$  with  $\rho(x) = \rho_0 \exp(-\frac{x}{L})$ .

Then we have

$$R_{TOT} = \int_{x=0}^{x=L} dR = \frac{1}{A} \int_0^L \rho_0 \exp\left(-\frac{x}{L}\right) dx$$

$$= \frac{\rho_0}{A} \left[ -L \exp\left(-\frac{x}{L}\right) \right]_0^L = \frac{\rho_0 L}{A} \left( 1 - \frac{1}{e} \right)$$

so (1)  $R_{TOT} = \frac{\rho_0 L}{A} \left( 1 - e^{-1} \right)$  (ans ✓)

Now suppose a potential difference of  $V$  is set up, so that  $\phi(0) = 0$  ~~( $\phi(x=c)$ )~~  
and  $\phi(x=L) = V$ .

By symmetry,  $\phi$  can only depend on  $x$ . Ohm's Law says,

$$(Q. 4.16) \quad \overline{J} = \frac{1}{\rho} \bar{E} = -\frac{1}{\rho} \nabla \phi. \quad \phi \text{ only depends on } x \Rightarrow \nabla \phi = \left( \frac{\partial \phi}{\partial x} \right) \hat{x}$$

and so, since the current must be constant in this resistor, we have  
(resistor insens)

$$\frac{1}{\rho} \frac{\partial \phi}{\partial x} = G = \text{constant.}$$

~~The last step~~ Then  $\frac{\partial \phi}{\partial x} = G \rho_0 \exp\left(-\frac{x}{L}\right)$

so that  $\phi(x) = A \exp\left(-\frac{x}{L}\right) + B$  where  $A, B$  are constants.




(3)

$$\begin{aligned}\phi(0) = 0 \Rightarrow A + B = 0 \\ \phi(L) = V \Rightarrow Ae^{-1} + B = V\end{aligned}\left.\right\} \Rightarrow \begin{aligned}(-B)e^{-1} + B = V \\ \Rightarrow B(1 - e^{-1}) = V \\ \Rightarrow B = \frac{V}{1 - e^{-1}} \quad \text{= crossed out}\end{aligned}$$

$(A = -B)$

Thus  $\boxed{\phi(x) = \frac{V}{1 - e^{-1}} \left(1 - \exp\left(-\frac{x}{L}\right)\right)}$

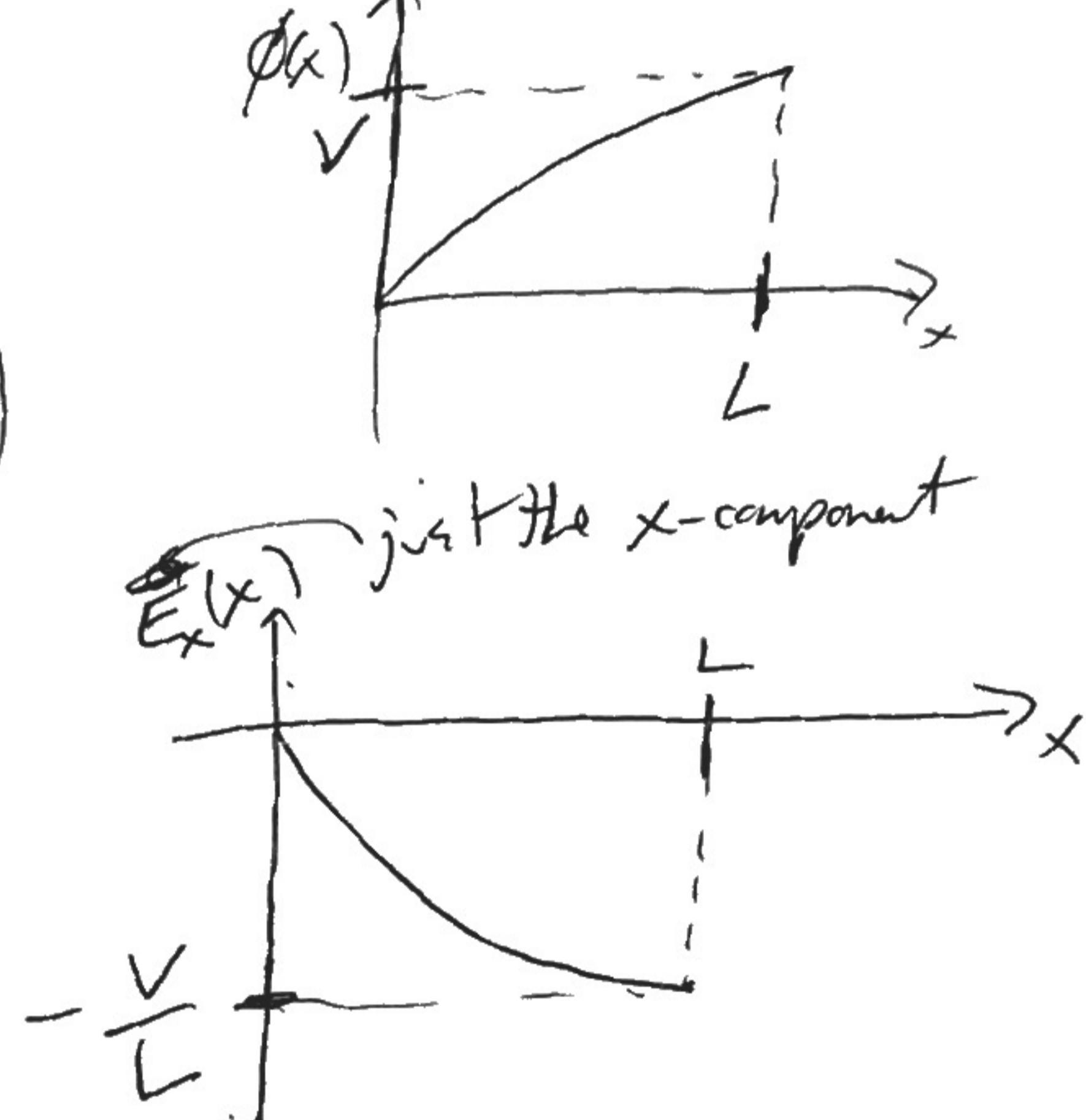$\boxed{E = -(\partial_x \phi)x = -\frac{V}{L(1 - e^{-1})} \left(1 - \exp\left(-\frac{x}{L}\right)\right)}$



#3) Pm 4.22 a) We have  $\rho = 3 \times 10^{-8}$  ohm-meter, each wire has diameter  $d = .73$  mm so that each wire's ~~crossed out~~ cross sectional area is  $A = \pi r^2 = \frac{\pi}{4} d^2$  and so the cross sectional area of the whole cable  $\phi$  (with 7 wires) is  $7A$ . ( $L = 3000$  km)

Thus  $R_{\text{tot}} = \rho \frac{L}{7A} = \cancel{0} \frac{3 \times 10^6 \cdot 3 \times 10^{-8}}{7 \cdot \frac{\pi}{4} \cancel{0} (.73 \times 10^{-3})^2} \approx 3.1 \times 10^4 \Omega$ .


$\therefore \boxed{R_{\text{tot}} \approx 3.1 \times 10^4 \Omega}$



(4)
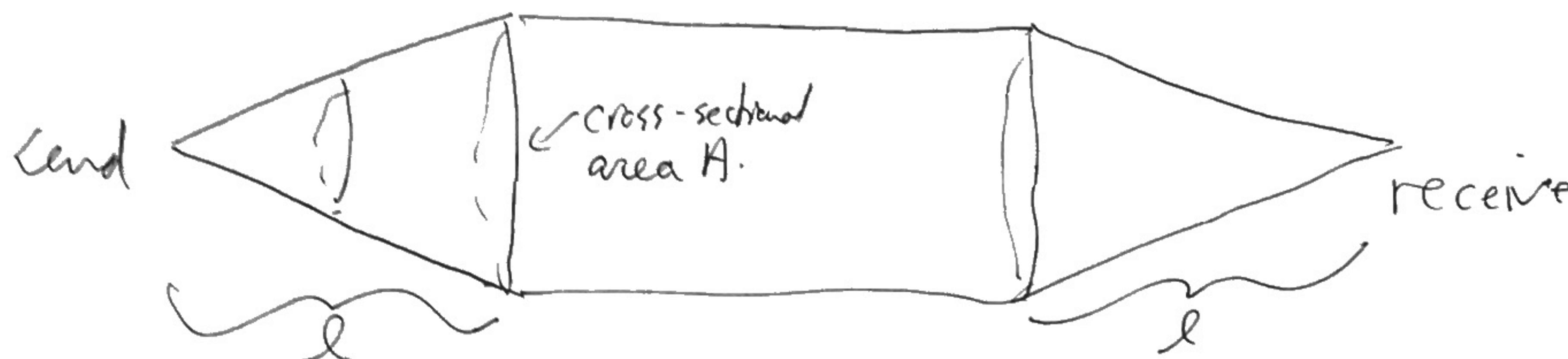
#3) (b) Let us assume the return path looks something like

$$\rho_{\text{water}} = .25 \text{ ohm-meter.}$$



We want an upper bound on the resistance of the return, so we can imagine the cross-sectional area  $A$  of the middle part is rather small (on oceanic scales), perhaps a radius of .5 km.

Then the resistance  $R_{\text{tube}}$  of the tubular part (even if we took its length to be the full 3,000 km) would be

$$R_{\text{tube}} = \frac{\rho L}{A} = \frac{.25 \cdot 3 \times 10^6}{\pi (.5 \times 10^3)^2} \approx 1 \Omega, \text{ which is tiny compared}$$

to what we got in part a).

~~Similarly, for the conic edges, we can break them up into cross-sectional circles. From radius 0 to radius .5 km, and thus (again taking each cone to have the full 3,000 km length (since after all, we just want an upper bound)) we get~~


~~$$R_{\text{cone}} = \rho \cdot l$$~~



(5)
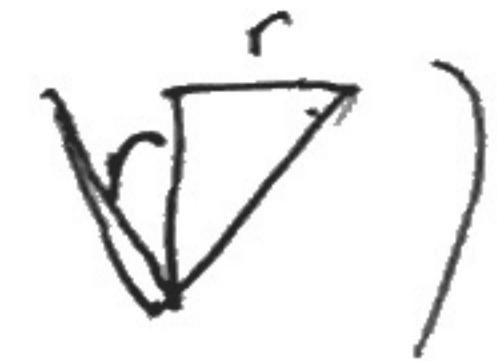
#3] (b) (cont'd)

(assume the cones are "right" cones, i.e.



Similarly, for the conic ends, we break  $R_{\text{cone}}$  up into circular cross-sections of length  $dr$  and cross-sectional area  $\pi r^2$ , and let us make the (generous) assumption that the initial radius is, say, .1 meter and the length of each cone is 1,000 km. (i.e.,  $1/3$  of the way across). After all, we just want an upper bound on  $R_{\text{TOT}}$ .

$$\text{We then have } R_{\text{cone}} = \rho \cdot \int_{r=0}^{r=1000\text{km}} \frac{dr}{\pi r^2} = \cancel{\rho} \frac{1}{\pi} \left( \frac{1}{.1\text{m}} - \frac{1}{10^6\text{m}} \right)$$

r=1,000km  
 length of each resistor  
 summing over all resistors  
 cross sectional area A

much smaller than first term,  
 so can drop it.


$$\text{so that } R_{\text{cone}} \approx \frac{10}{\pi} (.25) \Omega \text{m} \approx 1 \Omega.$$

Thus the total resistance  $R_{\text{TOT}} = R_{\text{tube}} + 2R_{\text{cone}}$  of the return is much smaller than the sending resistance,

(6)

#4) PM 4.35)


a)

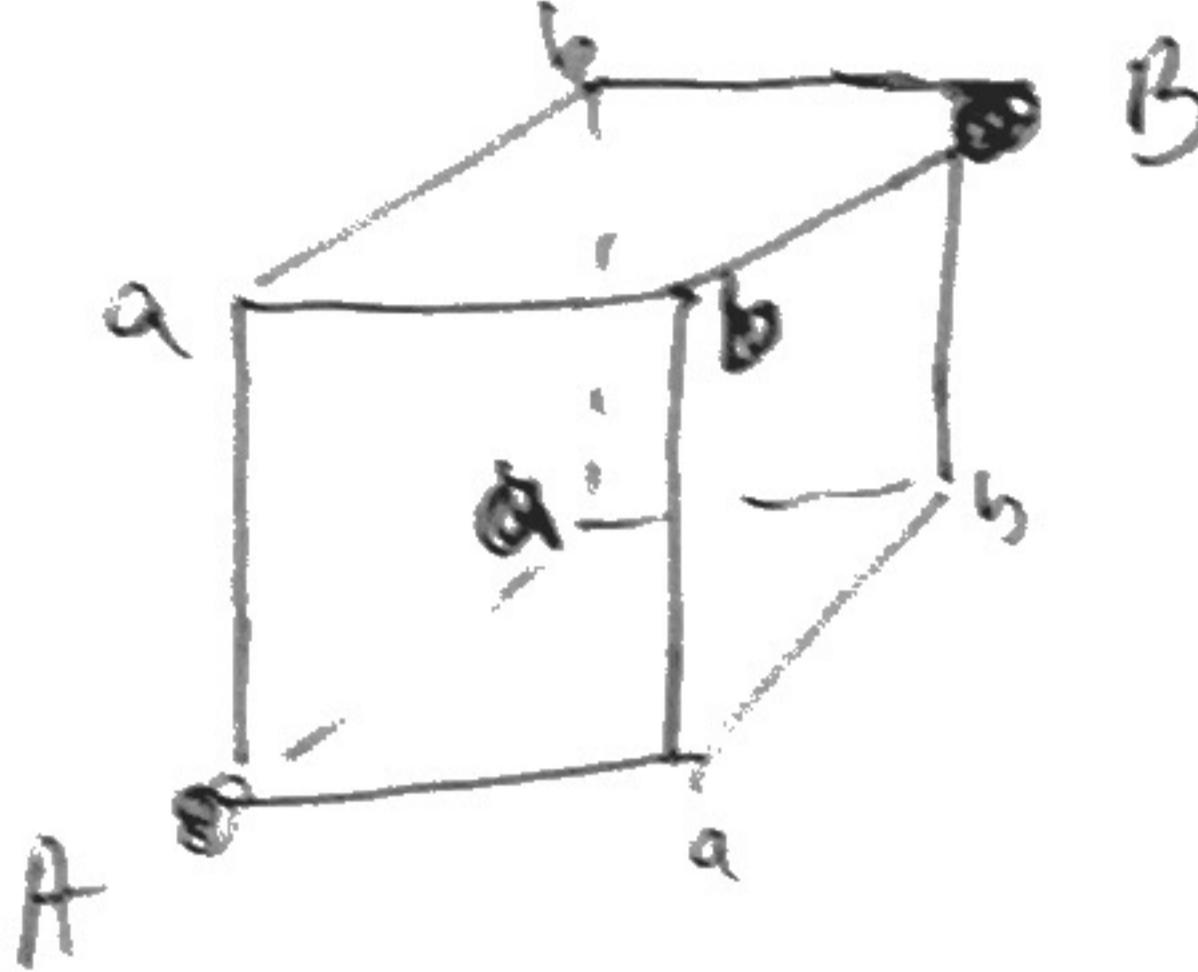

(rotational symmetry)

Due to ~~rotational symmetry~~, all the "a" vertices are at an equal potential, as are ~~the~~ the "b" vertices. Thus, shrinking these

down to points, we get

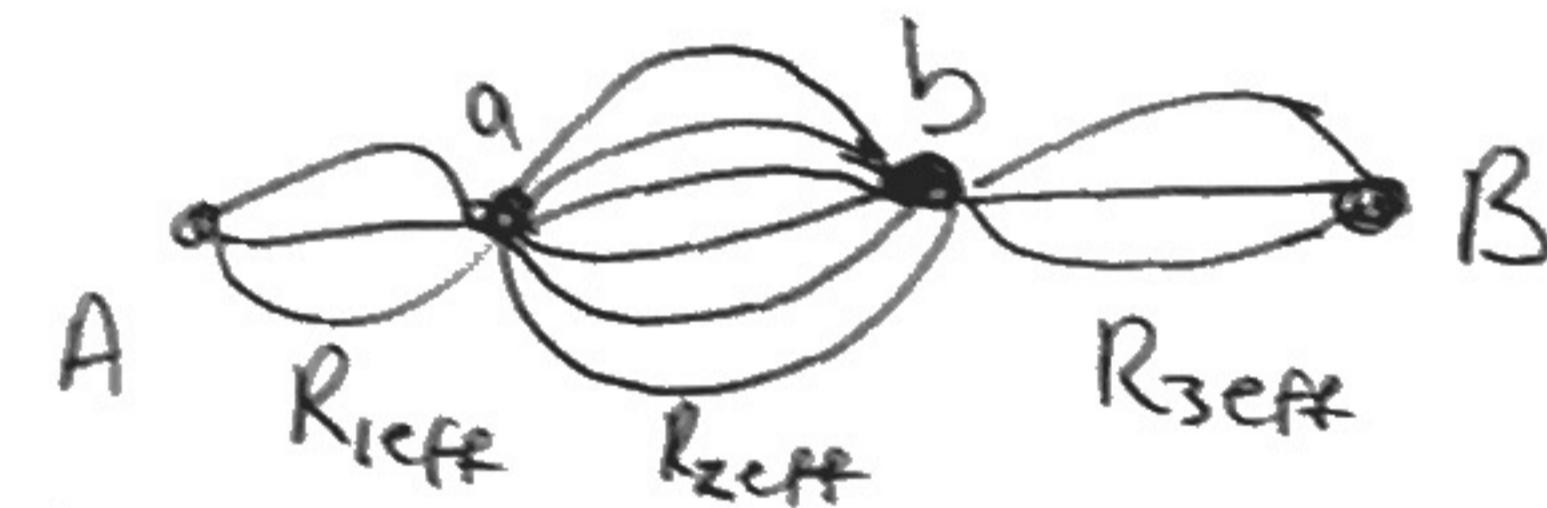


Since each line carries resistance  $R$ , we have  $R_{\text{eff}} = R_{3\text{eff}}$

and  $\frac{1}{R_{\text{eff}}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \Rightarrow R_{\text{eff}} = \frac{R}{3} = R_{3\text{eff}}$  and similarly  $R_{2\text{eff}} = \frac{R}{6}$ .

Thus


$$\boxed{R_{AB} = \frac{R}{3} + \frac{R}{6} + \frac{R}{3} = \frac{5}{6}R}$$

b)

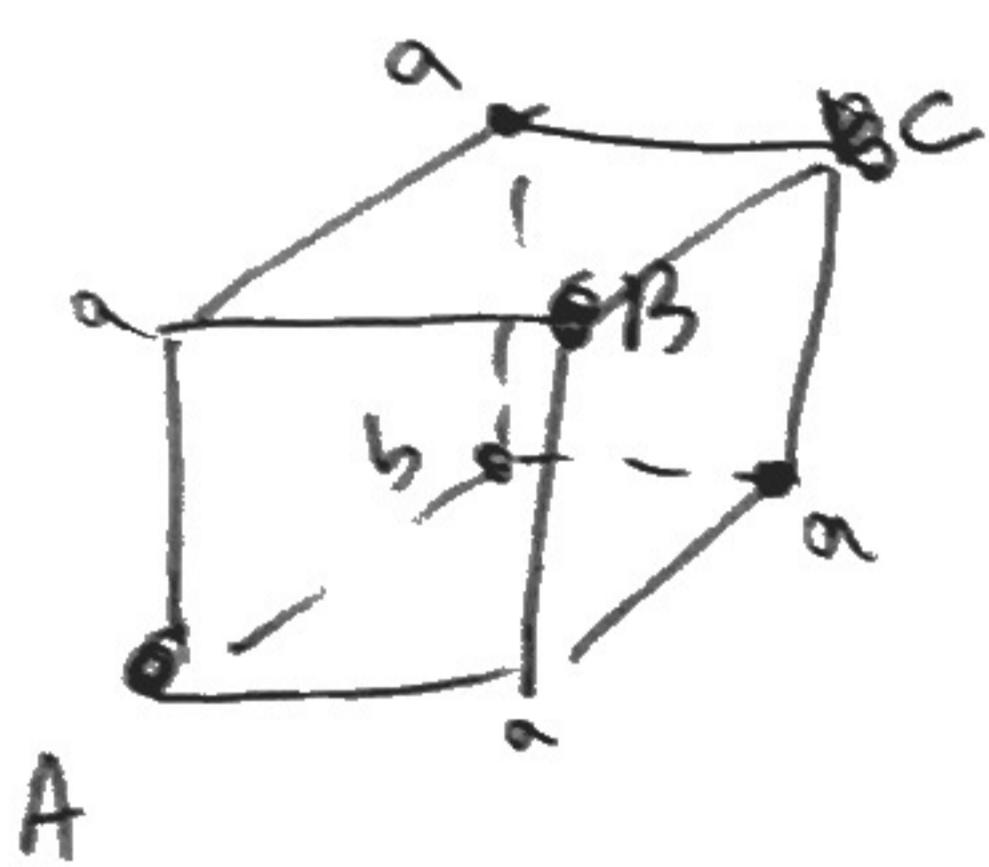


All "a" vertices are at equal potential since they lie on a plane equidistant from A and B

Shrinking piece down gives

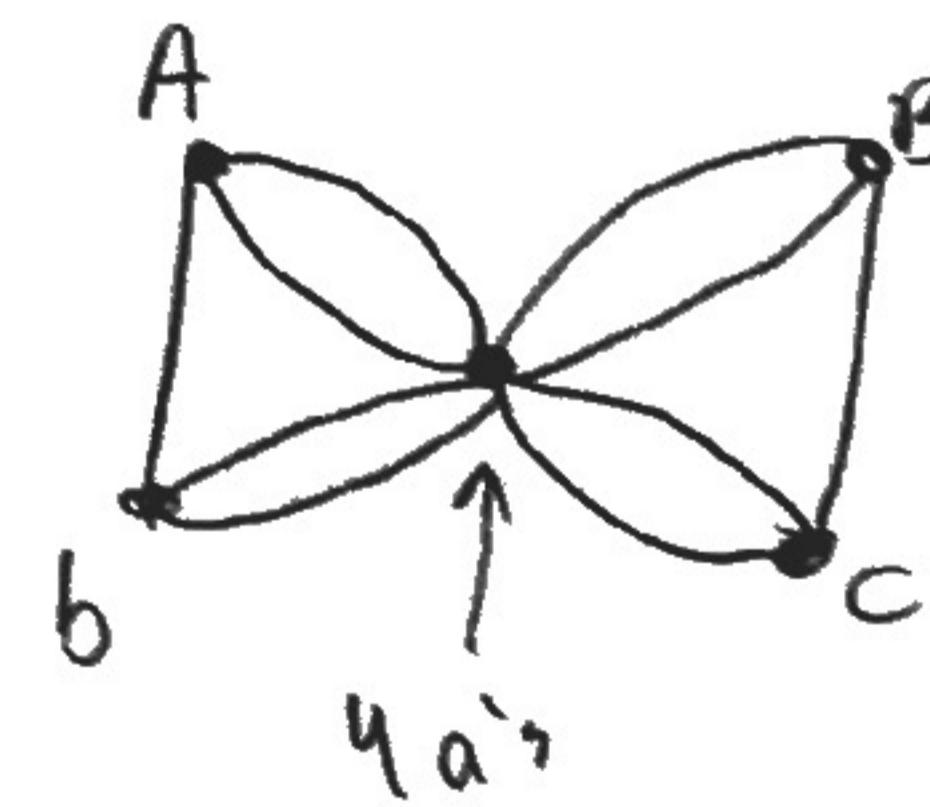

Note: we have lost two lines that connect the "a"s to each other.

This circuit is equivalent to

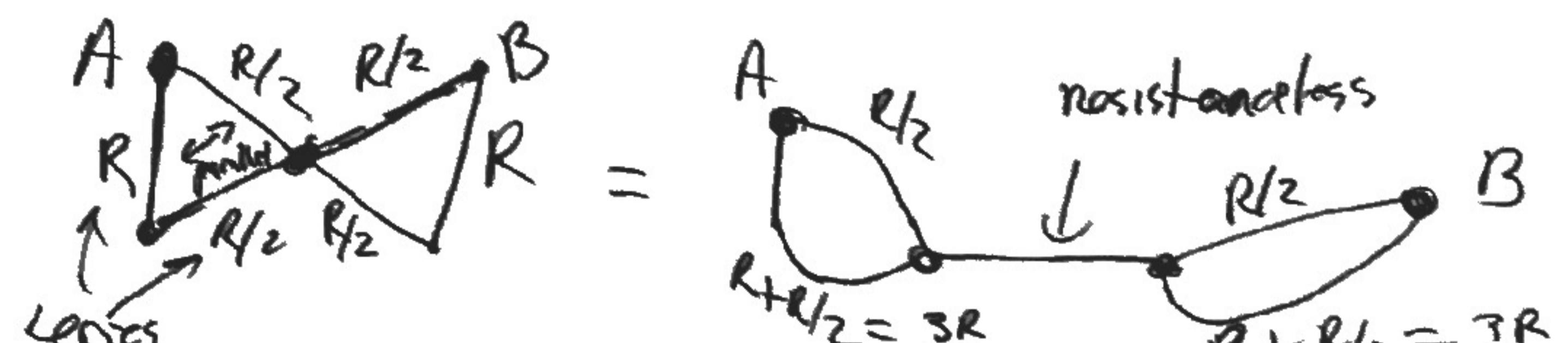

Note

where  $\frac{1}{R_{\text{eff}}} = \frac{2}{3R} + \frac{2}{R} = \frac{8}{3R} \Rightarrow R_{\text{eff}} = \frac{3R}{8}$

$= A \xrightarrow{\text{parallel}} \text{Neff} \xrightarrow{\text{parallel}} \text{Neff} \xrightarrow{\text{parallel}} B$


$= A \xrightarrow{\text{parallel}} \frac{1}{2R_{\text{eff}}} \xrightarrow{\text{parallel}} B$

Thus



$$\boxed{R_{AB} = \frac{3}{4}R}$$

(7)

#4]

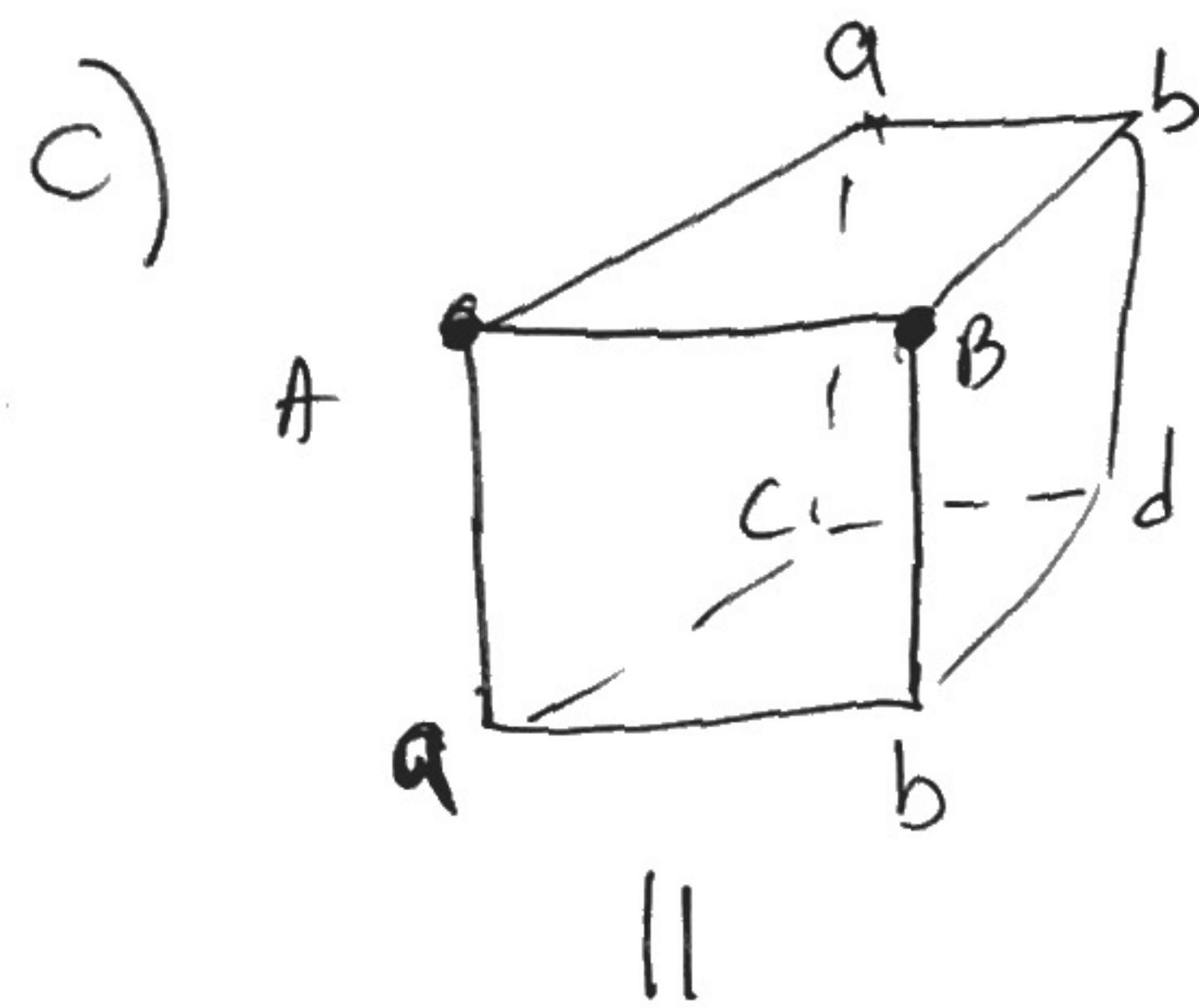

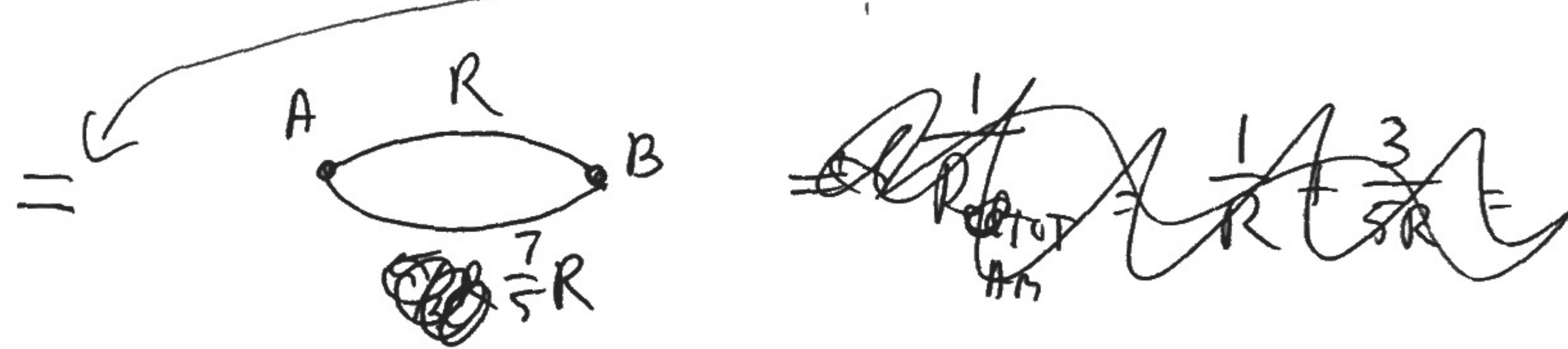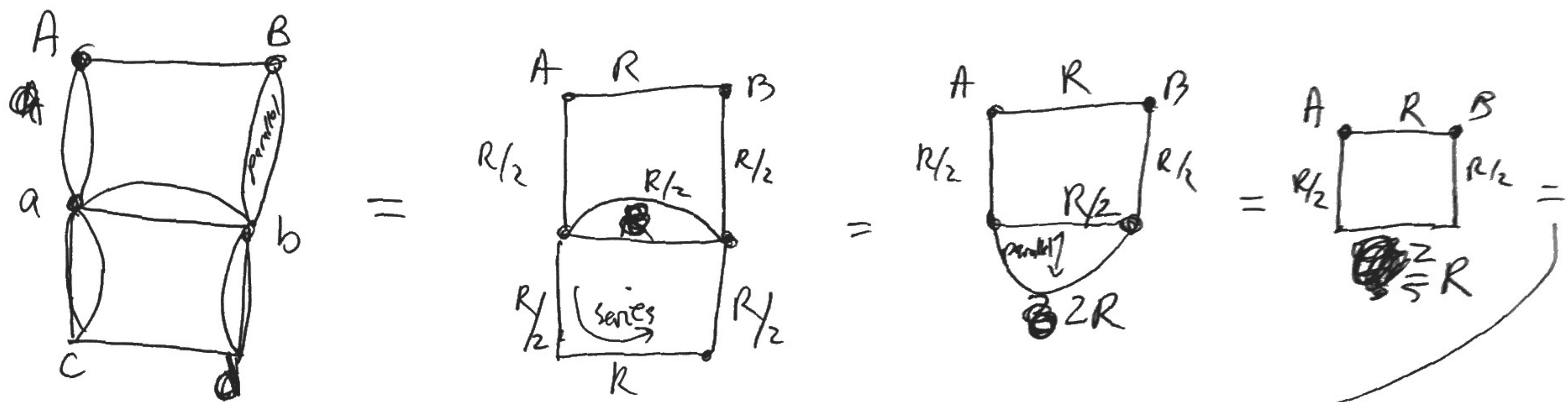
Similarly labelled vertices are at the same potential. For example, the 2 "a" vertices can be turned into each other via a rotation that keeps A and B fixed.



$$\Rightarrow \frac{1}{R_{\text{TOT}}} = \frac{1}{R} + \frac{5}{7R} = \frac{12}{7R} \Rightarrow \boxed{R_{\text{TOT}} = \frac{7R}{12}}$$


(8)

#5

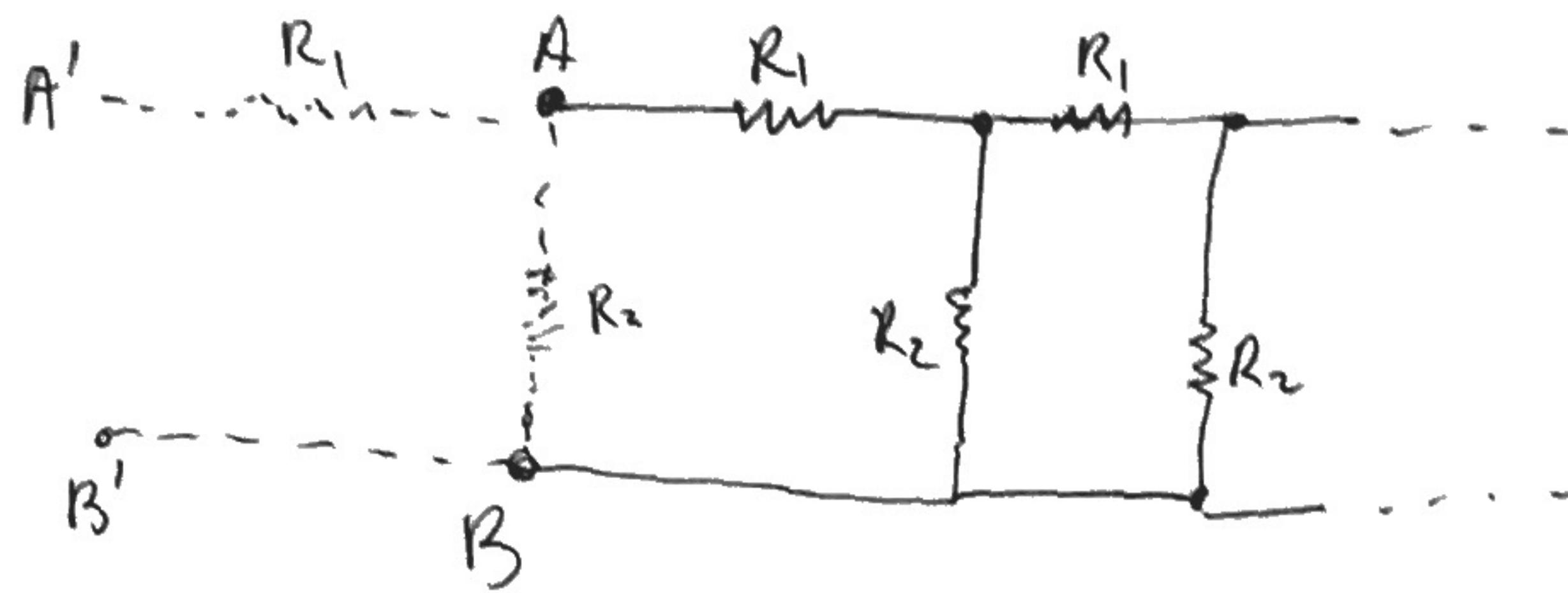

Let  $R$  be the total resistance of the full unit. By adding the suggested  $R_1$  and  $R_2$  (in dotted lines) we know we don't change the result.

But this addition is just

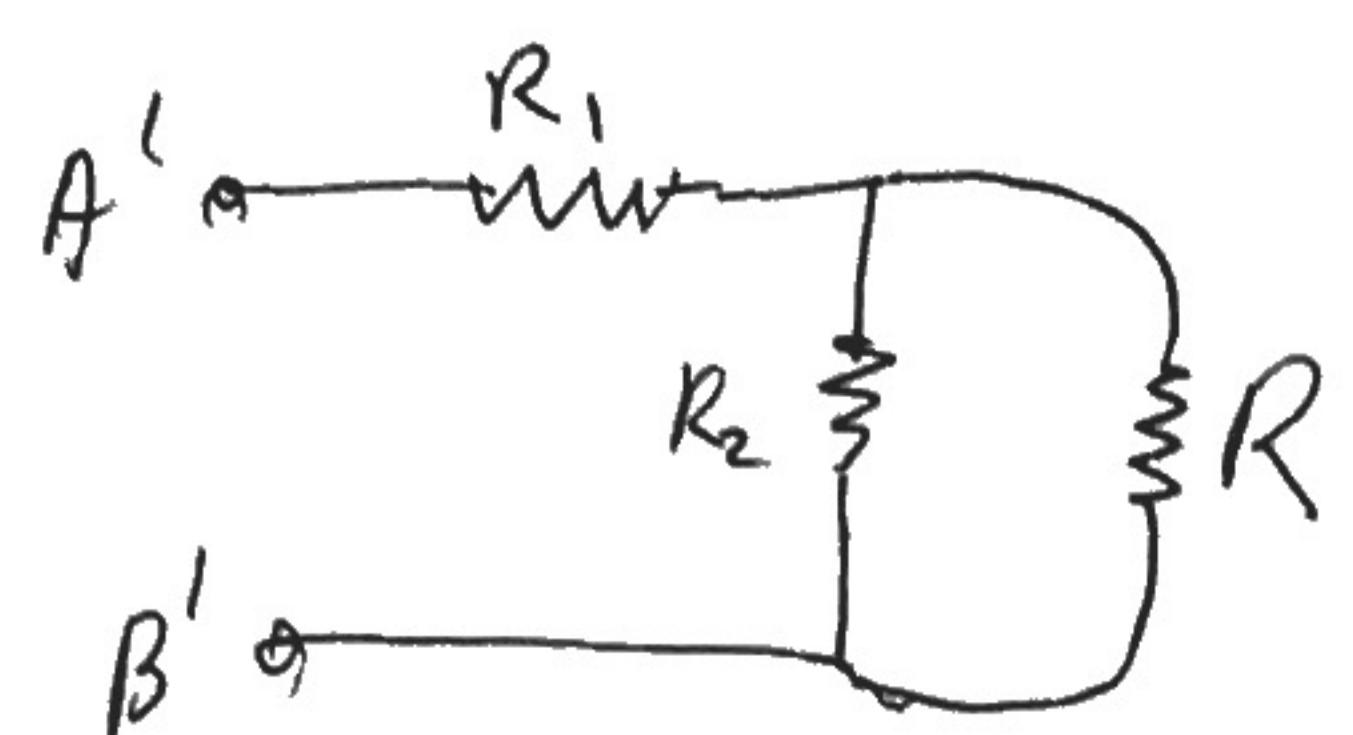

and the effective resistance  $R_{\text{eff}}$  (which we know is  $R$ ) is

$$R_{\text{eff}} = R = R_1 + \left( \frac{1}{\frac{1}{R} + \frac{1}{R_2}} \right) = R_1 + \frac{RR_2}{R+R_2}$$

Thus  $R = R_1 + \frac{RR_2}{R+R_2} \Rightarrow R(R+R_2) = R_1(R+R_2) + RR_2$



$$\Rightarrow R^2 + RR_2 = RR_1 + R_1R_2 + RR_2 \Rightarrow R^2 - R_1R_2 - R_1R_2 = 0$$

$$\Rightarrow R = \frac{1}{2} \left( R_1 \pm \sqrt{R_1^2 + 4R_1R_2} \right) \quad (\text{only take positive value}).$$

so 
$$R = \frac{1}{2} \left( R_1 + \sqrt{R_1^2 + 4R_1R_2} \right)$$

9
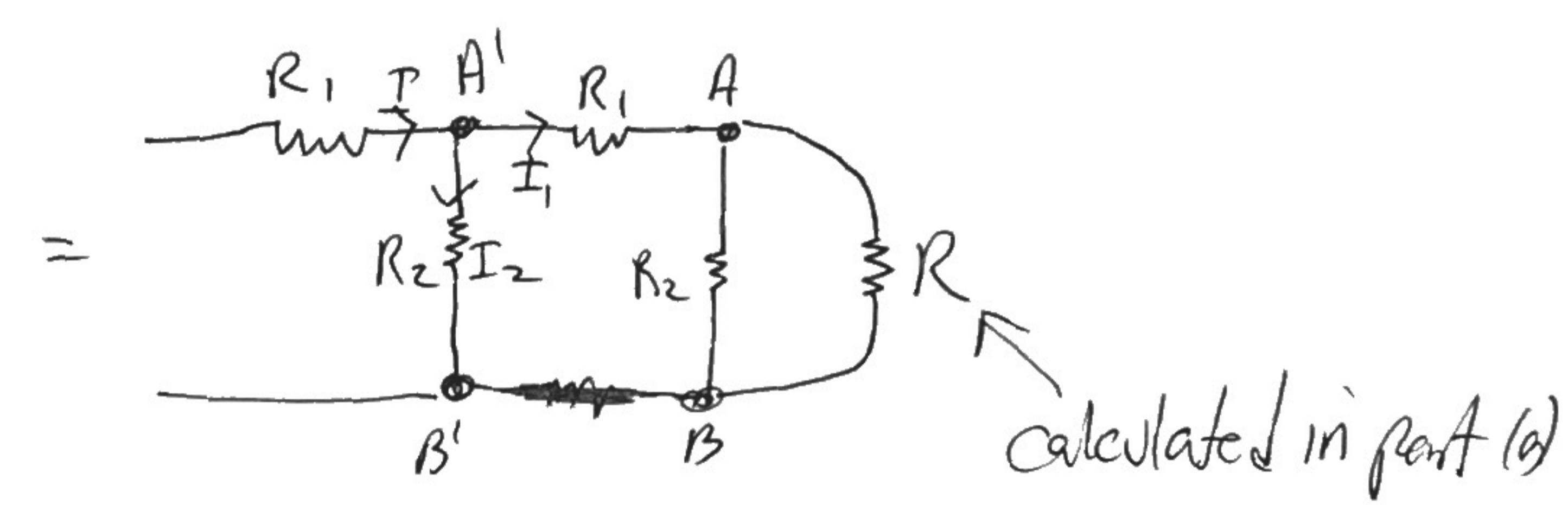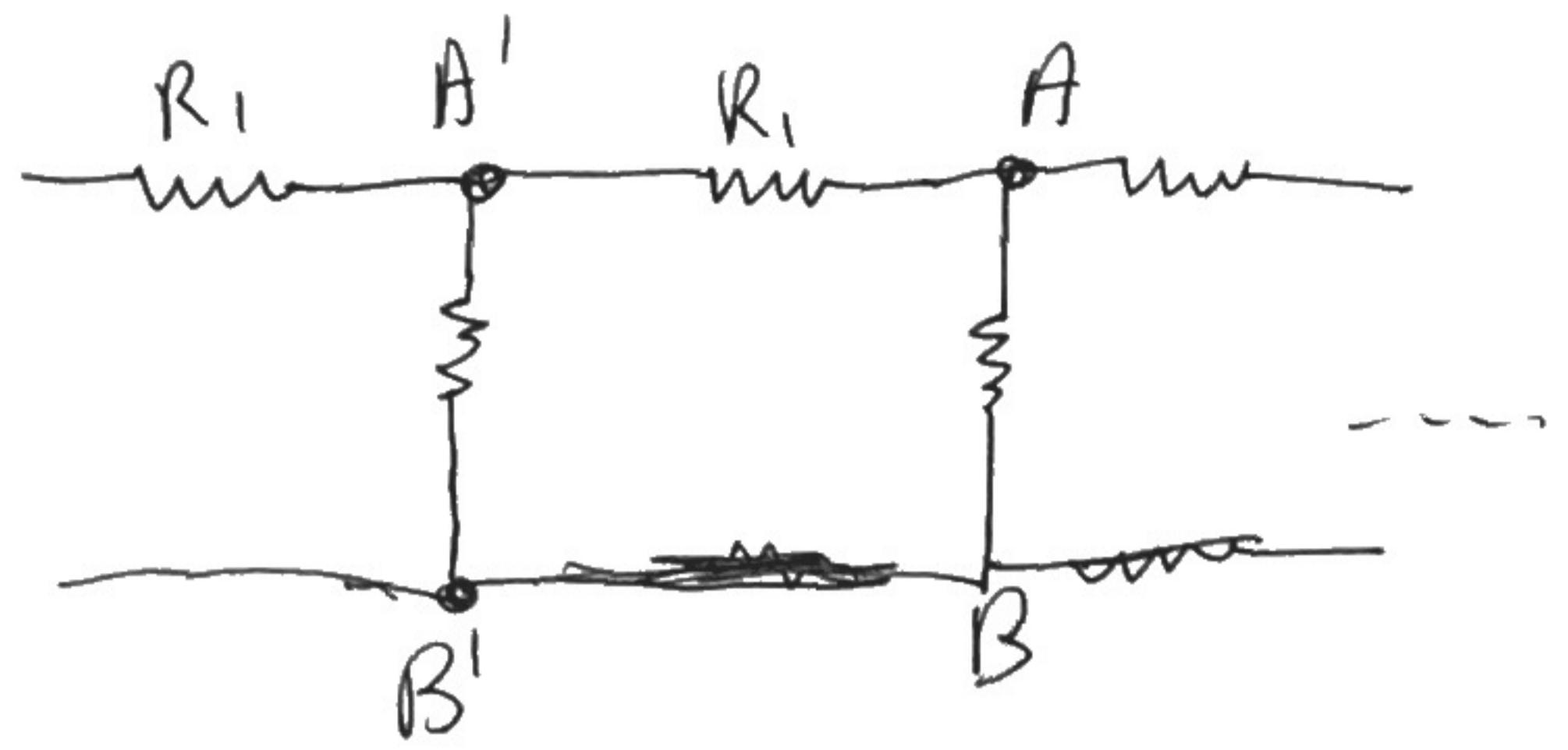
#5] (cont'd) Now consider a square somewhere in the circuit (with corners  $A, A', B, B'$ ):



with current  $I$  going into  $A'$  and  $I_1, I_2$  as shown, so that in particular  $I_1 + I_2 = I$ . Now, the effective resistance between  $A$  and  $B$

is  $\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{\text{eff}} = \frac{R_1 R_2}{R_1 + R_2}$ , so that the voltage drop  $V_{AB}$

between  $A$  and  $B$  is  $V_{AB} = I_1 \left( \frac{R_1 R_2}{R_1 + R_2} \right)$ . However, the circuit to the right of  $A'$  and  $B'$  is also just an effective resistor with resistance  $R$  (even though it has an extra  $R_1 + R_2$  attached (recall part (a))). Thus the effective resistance between  $A'$  and  $B'$  is also  $\frac{R_1 R_2}{R_1 + R_2}$  so that the voltage difference  $V_{A'B'}$

between  $A'$  and  $B'$  is  $V_{A'B'} = I \frac{R_1 R_2}{R_1 + R_2}$ . Thus,

$$\frac{V_{AB}}{V_{A'B'}} = \frac{I_1 \left( \frac{R_1 R_2}{R_1 + R_2} \right)}{I \left( \frac{R_1 R_2}{R_1 + R_2} \right)} = \frac{I_1}{I}.$$

Now, since the circuit to the right of  $A'$  and  $B'$  is just a resistor  $R$ , we have that  $I_1 R = I_2 R_2$ . This with  $I_1 + I_2 = I \Rightarrow I_1 + I_1 \frac{R}{R_2} = I \Rightarrow I_1 = \frac{I}{1 + \frac{R}{R_2}}$ .

Thus  $\boxed{\frac{V_{AB}}{V_{A'B'}} = \frac{R_2}{R_2 + R}}$  if we want  $\frac{V_{AB}}{V_{A'B'}} = \frac{1}{2}$  then we take  $R = R_2$ ,

so that, from (a), we have  $R_2 = R = \frac{1}{2}(R_1 + \sqrt{R_1^2 + 4R_1 R_2})$   ~~$\rightarrow R_2 = \sqrt{R_1^2 + 4R_1 R_2}$~~

~~$R = R_1 + R_2$~~



(10)

This gives

$$2R_2 = R_1 + \sqrt{R_1^2 + 4R_1R_2}$$


$$\Rightarrow (2R_2 - R_1)^2 = R_1^2 + 4R_1R_2 \Rightarrow 4R_2^2 + R_1^2 - 4R_1R_2 = R_1^2 + 4R_1R_2$$

Don't cancel  
(typo)


$$\Rightarrow R_2^2 = 2R_1R_2 \Rightarrow \boxed{R_2 = 2R_1}$$

To emulate an infinite ladder with finitely many resistors, we simply need to cut the ladder off and attach a resistor with value  $R = \frac{1}{2} (R_1 + \sqrt{R_1^2 + 4R_1R_2})$  in parallel with an  $R_2$ .

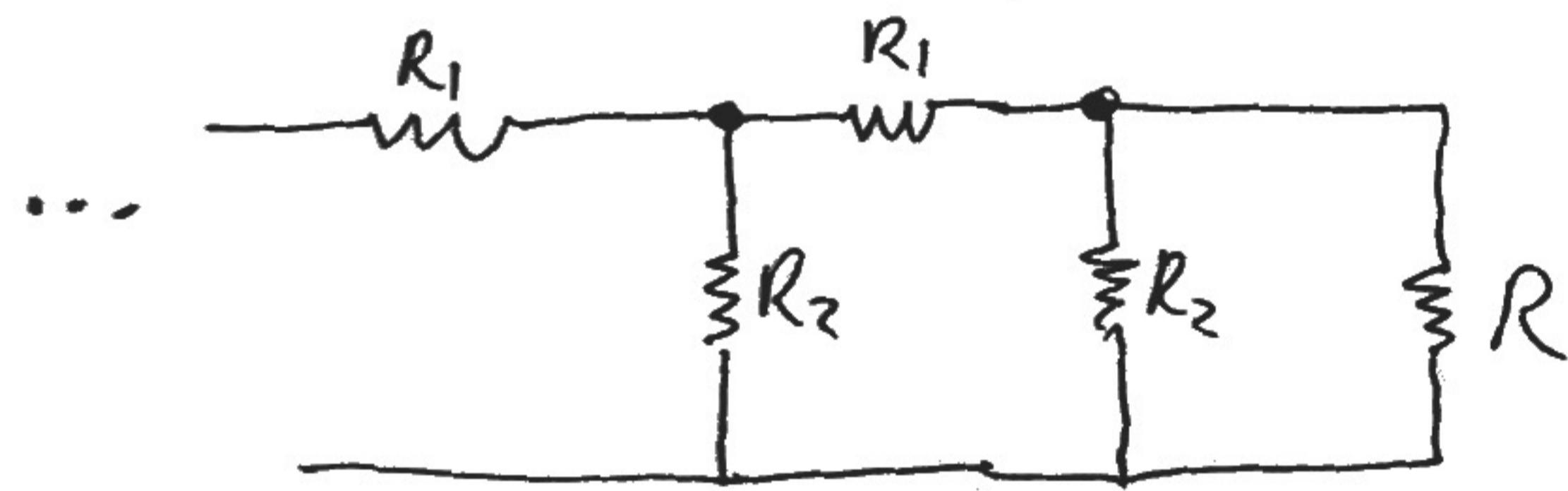Namely, as shown on the right of the top of the previous page we can use



#6) PM 9.40

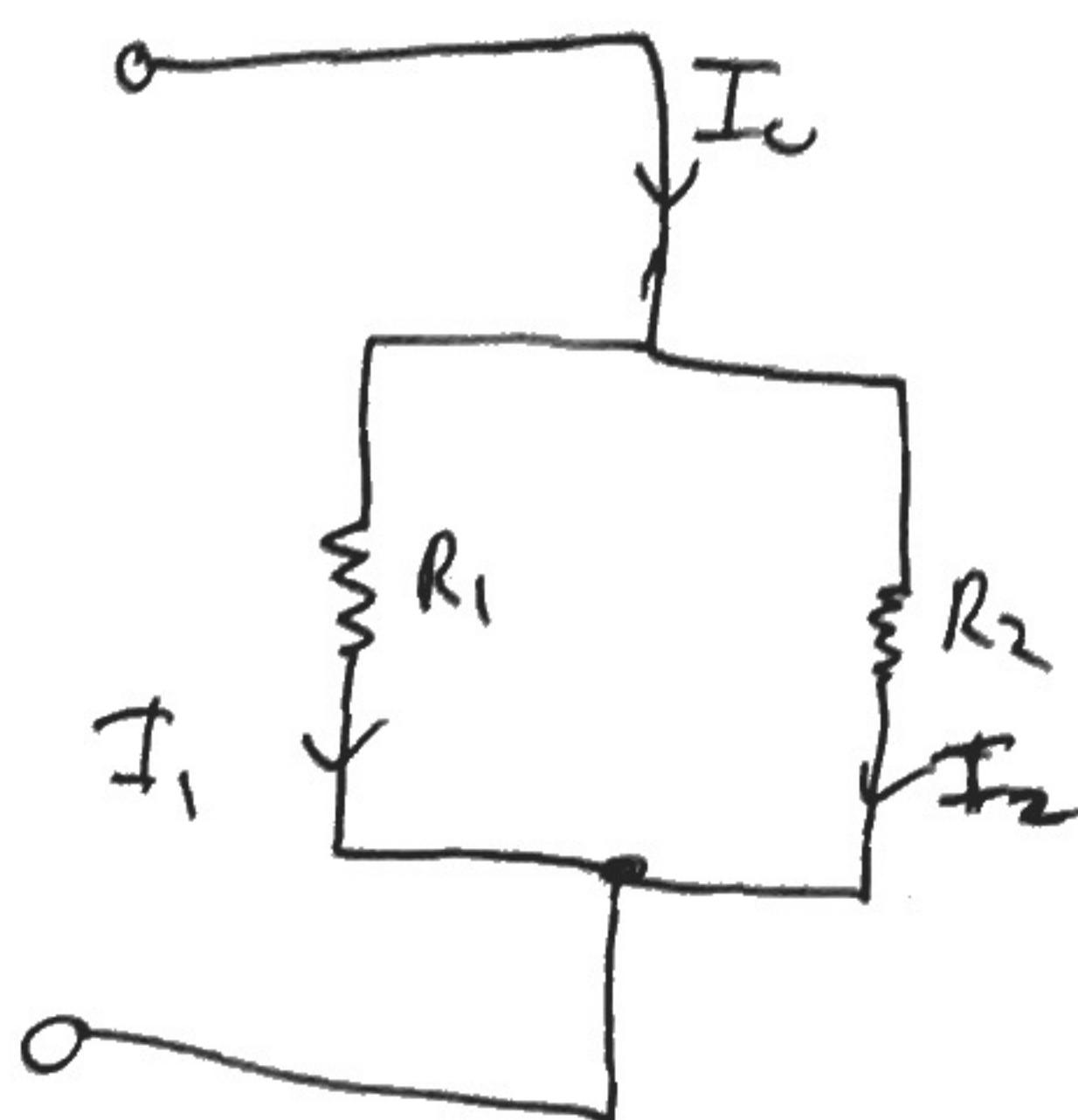

The total power dissipated is  $P_{\text{tot}} = I_1^2 R_1 + I_2^2 R_2$ . Using  $I_2 = I_o - I_1$  gives

$$\begin{aligned} P_{\text{tot}} &= I_1^2 R_1 + (I_o - I_1)^2 R_2 \\ &= I_1^2 R_1 + I_o^2 R_2 - 2 I_o I_1 R_2 + I_1^2 R_2 \\ &= I_o^2 R_2 + I_1^2 (R_1 + R_2) - 2 I_o I_1 R_2. \end{aligned}$$

Minimizing this ~~for  $I_1$~~  with respect to  $I_1$  gives

$$0 = \frac{dP_{\text{tot}}}{dI_1} = 2 I_1 (R_1 + R_2) - 2 I_o R_2 \Rightarrow \boxed{I_1 = \frac{R_2}{R_1 + R_2} I_o}$$

just as we expect.

Ex 4.48 we first do problem 4.17:



Kirchoff's 1st law, after the switch is closed, tells us that  $V - \frac{Q}{C} - IR = 0$ .

voltage drop across capacitor

$$\Rightarrow IR = \frac{Q}{C} - V.$$

$$I = \frac{dQ}{dt} \Rightarrow \frac{dQ}{dt} = \frac{Q}{RC} - V. \quad (\text{as can/should be checked})$$

This equation has the standard solution  $Q(t) = CV(1 - e^{-t/RC})$

(to "derive" this, try  $Q(t) = A(1 - e^{-t/\tau})$  and solve for  $\tau$ ,  $A$  by differentiating and also requiring  $Q(t \rightarrow \infty) = CV$ , as we know it should). (Note: we guess the because we want  $Q(0) = 0$ )

Then we see that  $I(t) = \frac{dQ}{dt} = \frac{V}{R} e^{-t/RC}$ . ( $Q = CV$ )

Now, the work done by the battery in charging up the capacitor is  $W_{\text{battery}} = QV = CV^2$  since it must move a total charge of  $Q = CV$  against the constant potential  $V$ . So  $W_{\text{battery}} = CV^2$ .

The final energy stored in the ~~battery~~ ~~Capacitor~~ Capacitor is of course  $E_{\text{capacitor}} = \frac{1}{2}CV^2$ .


And the total power dissipated  $U_{\text{dissipated}} = \int_{t=0}^{\infty} I^2 R dt = \frac{V^2}{R} \int_{t=0}^{\infty} e^{-2t/RC} dt = -\frac{RC}{2R} V^2 e^{-2t/RC} \Big|_0^{\infty}$

so that  $U_{\text{dissipated}} = \frac{1}{2}CV^2$ .

Indeed,  $W_{\text{battery}} = CV^2 = U_{\text{dissipated}} + E_{\text{capacitor}} = \frac{1}{2}CV^2 + \frac{1}{2}CV^2$ , as desired.

(13)

#8]

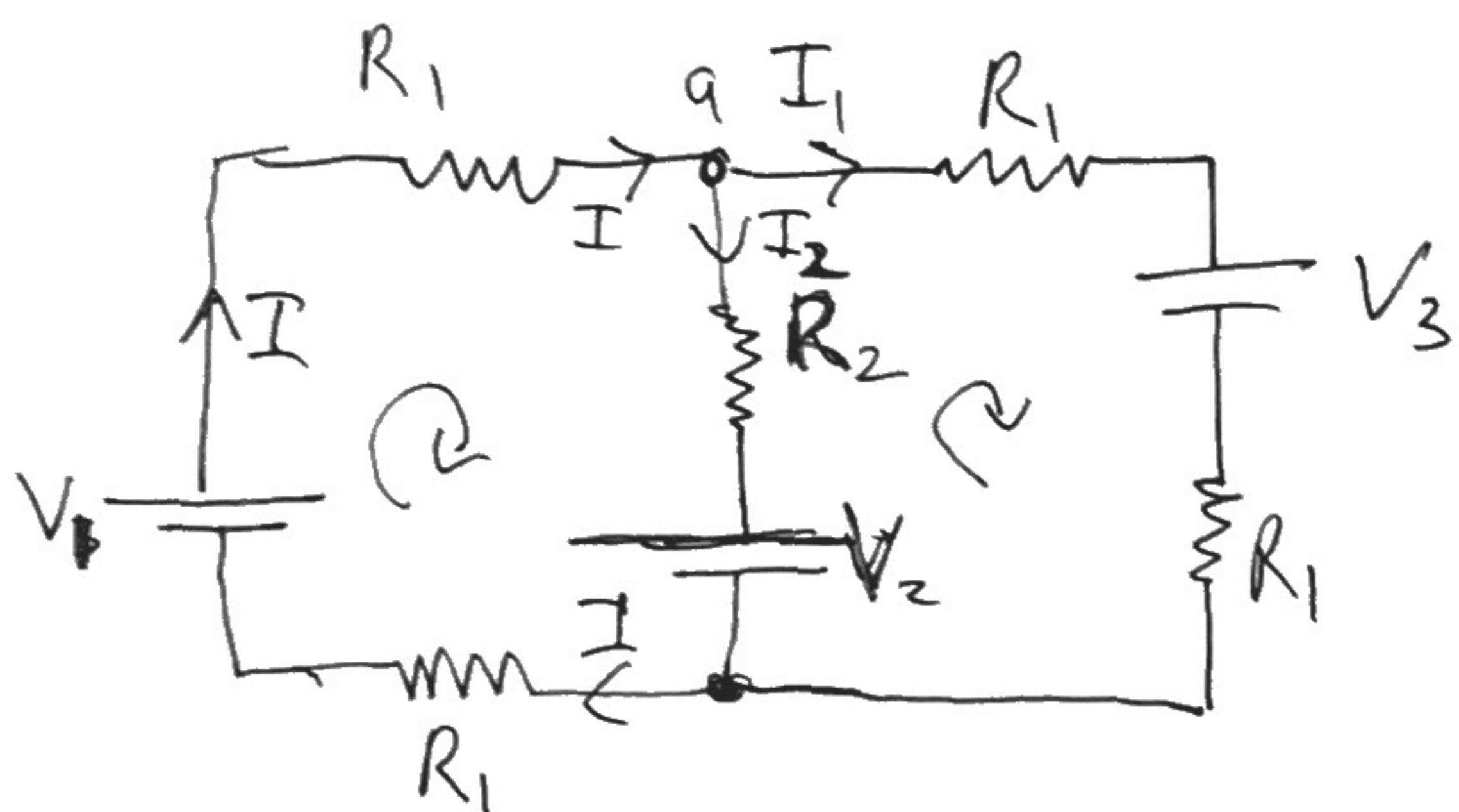

$$R_1 = 1 \Omega$$

$$R_2 = 2 \Omega$$

~~$$V_2 = V_3 = 4 \text{ Volts}$$~~

$$V_1 = 2 \text{ Volts}$$

Equations:  $I_1 + I_2 = I$  (\*)

Kirchhoff on RHS  $\Rightarrow -I_2 R_2 - V_2 = -I_1 R_1 - V_3 - I_1 R_1$

$$\Rightarrow I_2 R_2 + V_2 = 2I_1 R_1 + V_3$$

$$\Rightarrow I_2 R_2 = 2I_1 R_1 \quad (\text{since } V_2 = V_3)$$

Since  $R_2 = 2R_1$

$$\Rightarrow 2I_2 = 2I_1 \Rightarrow I_1 = I_2.$$
~~$$I_1 = I_2 = \frac{I}{2}$$~~

Kirchhoff on LHS:  $V_0 - IR_1 - I_2 R_2 - V_2 - IR_1 = 0$

~~$$IR_1 = I_2 R_2$$~~

$$\Rightarrow -2IR_1 + V_1 - V_2 = I_2 R_2$$

$$\Rightarrow -2IR_1 = I_2 R_2 + 2 \quad \Rightarrow -2I = 2I_2 + 2$$

$$\Rightarrow -I = \frac{I_2}{2} + 1 \Rightarrow -\frac{3}{2}I = 1 \Rightarrow I = -\frac{2}{3} \text{ Amps.}$$

Thus  $I$  actually goes down with  $\frac{2}{3}$  Amps.

so  $I_1$  goes up with  $\frac{1}{3}$  Amps, as does  $I_2$  (up with  $\frac{1}{3}$  Amps)

$$V_{ab} = -I_2 R_2 + V_2 = \left(-\frac{1}{3}\right) \cdot 2 + 4 \text{ Volts} = \frac{10}{3} \text{ Volts.}$$

$$V_{ab} = \frac{10}{3} \text{ Volts}$$