

Problem Set #9 Solutions (Last two problems)

(1)

(The rest have answers in
the back)

#1) PM #8.17 After Q cycles, the angle ωt is equal to $2\pi \cdot Q$ radians (just the usual cycles \Rightarrow radians conversion). Using equation (8.13) we have $Q = \frac{\omega}{2\alpha}$, thus


$$2\pi Q = 2\pi \cdot \frac{\omega}{2\alpha} = \pi \frac{\omega}{\alpha} = \omega t. \text{ Thus, it takes } \cancel{2\pi Q}$$

$t = \frac{\pi}{\alpha}$ seconds to go Q cycles.


Since both $I(t)$ and $V(t)$ go as $e^{-\alpha t}$, we have after Q cycles (or $t = \frac{\pi}{\alpha}$ seconds) that $I(t)$ and $V(t)$ have decreased by $e^{-\alpha(\frac{\pi}{\alpha})} = e^{-\pi}$, as desired.

#2) PM #8.33

Box 1:

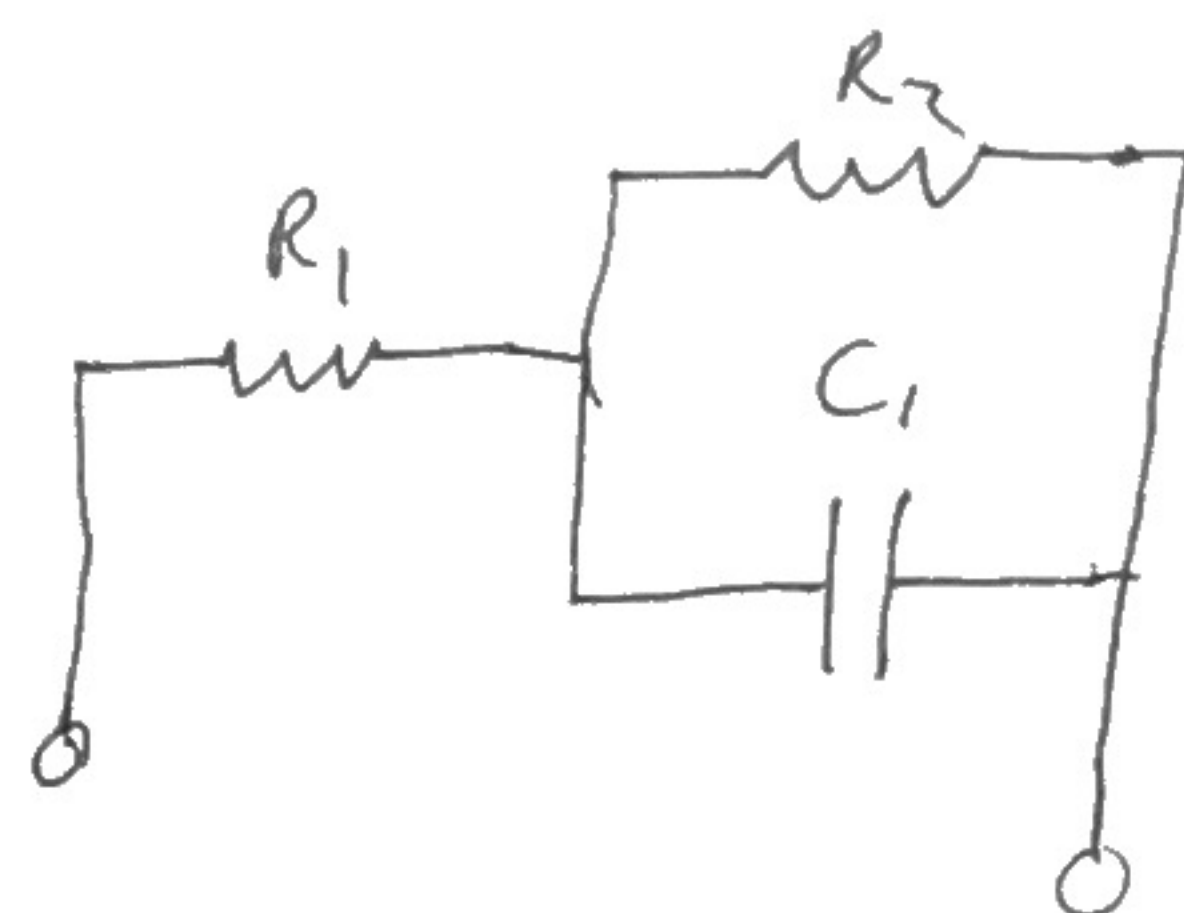

Box 2:

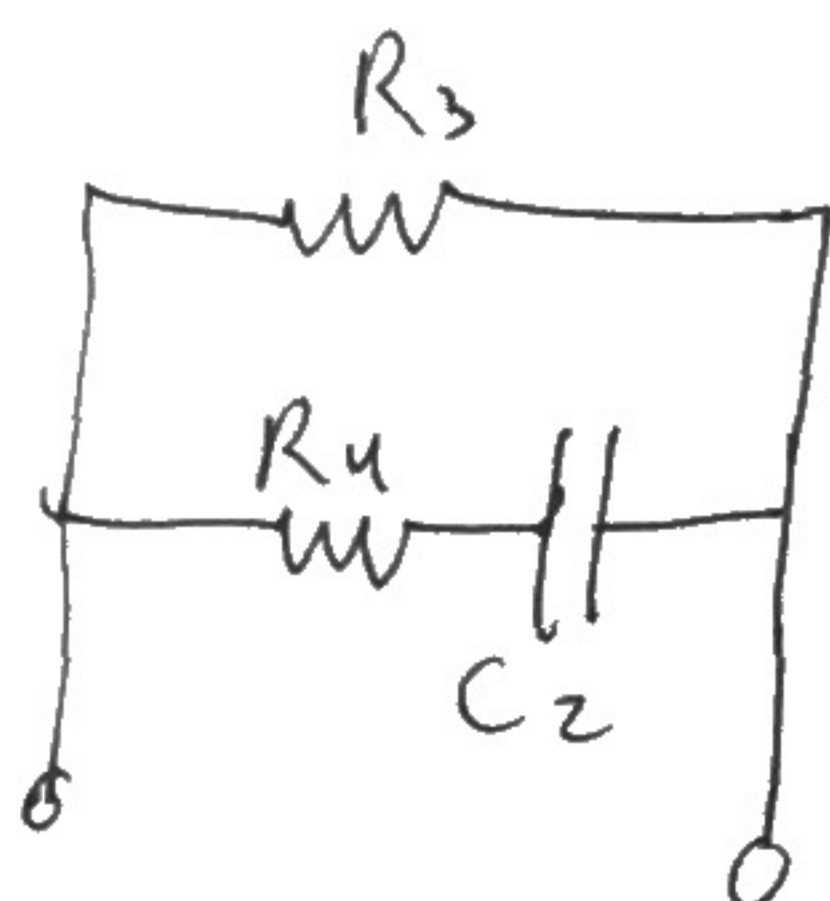

$$R_1 = 1000 \Omega, R_2 = 4000 \Omega, C_1 = 1 \mu F$$

$$R_3 = 5000 \Omega, R_4 = 1250 \Omega, C_2 = .6 \mu F$$

For box 1: R_1 in series with $R_2 \parallel C_1$.

Recall: $Z_C = \frac{1}{i\omega C}$
 impedance for capacitor

$Z_R = R$
 for resistor

just like normal resistors

$$\text{so } \frac{1}{Z_{R_2 \parallel C_1}} = \frac{1}{Z_{R_2}} + \frac{1}{Z_{C_1}} \Rightarrow Z_{R_2 \parallel C_1} = \frac{Z_{R_2} Z_{C_1}}{Z_{R_2} + Z_{C_1}} = \frac{R_2}{i\omega C R_2 + 1} = \frac{R_2}{1 + i\omega C R_2}$$

$$\text{so } Z_{\text{eff } 1} = Z_{R_1} + Z_{R_2 \parallel C_1} = R_1 + \frac{R_2}{1 + i\omega C R_2} = R_1 + \frac{R_2(1 - i\omega C R_2)}{1 + \omega^2 C^2 R_2^2}$$

$$= \frac{(R_1 + R_2) + C_1^2 R_2^2 R_1 \omega^2 - i C_1 R_2^2 \omega}{1 + \omega^2 C_1^2 R_2^2}$$

plugging in numbers

$$\Rightarrow Z_{\text{eff } 1} = \frac{5000 + 16 \times 10^{-3} \omega^2 - 16i\omega}{1 + 16 \times 10^{-6} \omega^2}$$

as desired.

Similar $Z_{\text{eff } 2} = Z_{R_3} \parallel \underbrace{(Z_{R_4} + Z_{C_2})}_{\text{series}}$
 For box 2 parallel

using $Z_1 \parallel Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$

$$\Rightarrow \frac{Z_{R_3} (Z_{R_4} + Z_{C_2})}{Z_{R_3} + Z_{R_4} + Z_{C_2}} = \frac{R_3 (R_4 + \frac{1}{i\omega C_2})}{R_3 + R_4 + \frac{1}{i\omega C_2}}$$

multiply by $i\omega C_2$ on top and bottom

$$\Rightarrow \frac{R_3 + i\omega C_2 R_3 R_4}{1 + i\omega C_2 (R_3 + R_4)} = \frac{(R_3 + i\omega C_2 R_3 R_4)(1 - i\omega C_2 (R_3 + R_4))}{1 + \omega^2 C_2^2 (R_3 + R_4)^2}$$

(*)

$$\frac{R_3 + C_2^2 R_3 R_4 (R_3 + R_4) \omega^2 - C_2 R_3^2 \omega i}{1 + C_2^2 (R_3 + R_4)^2 \omega^2}$$

plugging in numbers

$$\Rightarrow Z_{\text{eff } 2} = \frac{5000 + 16 \times 10^{-3} \omega^2 - 16i\omega}{1 + 16 \times 10^{-6} \omega^2}$$

as desired

Now, to get R_3, R_4 , and C_2 from a given R_1, R_2 and C_1 with the constraint that $Z_{\text{eff } 1} = Z_{\text{eff } 2}$ for all ω , we explore (from page (2) and (*) on this page)

$$Z_{\text{eff } 1} = Z_{\text{eff } 2} \Rightarrow \frac{(R_1 + R_2) + C_1^2 R_2^2 R_1 \omega^2 - i C_1 R_2 \omega}{1 + \omega^2 C_1^2 R_2^2} = \frac{R_3 + C_2^2 R_3 R_4 (R_3 + R_4) \omega^2 - C_2 R_3^2 \omega i}{1 + C_2^2 (R_3 + R_4)^2 \omega^2}$$

By clearing denominators and bringing all the terms together we get 50 different powers of ω : the 0th power, ω^3 , and ω^4

(4)

Now, to get R_3, R_4 , and C_2 from R_1, R_2 and C_1 , ~~we~~ subject to the constraint that $Z_{\text{eff}1} = Z_{\text{eff}2}$, ~~and~~ we need to explore

$$Z_{\text{eff}1} = R_1 + \frac{1}{\frac{1}{R_2} + i\omega C_1} = \frac{1}{\frac{1}{R_3} + \frac{1}{R_4 + \frac{1}{i\omega C_2}}}$$

$Z_{R_1} + \underbrace{\left(\frac{1}{\frac{1}{Z_{R_2}} + \frac{1}{Z_{C_1}}} \right)}_{Z_{R_2 \parallel C_1}}$

$$\Rightarrow \left(\frac{1}{R_3} + \frac{1}{R_4 + \frac{1}{i\omega C_2}} \right) \left(R_1 + \frac{1}{\frac{1}{R_2} + i\omega C_1} \right) = 1$$

$$\Rightarrow \left(\frac{1}{R_3} + \frac{1}{R_4 + \frac{1}{i\omega C_2}} \right) \left(\frac{R_1/R_2 + i\omega C_1 R_1 + 1}{\frac{1}{R_2} + i\omega C_1} \right) = 1$$

$$\Rightarrow \left(\frac{R_4 + \frac{1}{i\omega C_2} + R_3}{R_3(R_4 + \frac{1}{i\omega C_2})} \right) \left(\frac{R_1}{R_2} + i\omega C_1 R_1 + 1 \right) = \frac{1}{R_2} + i\omega C_1$$

$$\Rightarrow \left(1 + \frac{R_4}{R_3} + \frac{1}{i\omega C_2 R_3} \right) \left(\frac{R_1}{R_2} + i\omega C_1 R_1 + 1 \right) = \left(\frac{1}{R_2} + i\omega C_1 \right) \left(R_4 + \frac{1}{i\omega C_2} \right)$$

multiply by $i\omega C_2 R_3$ $\Rightarrow (1 + i\omega C_2 R_3 + i\omega C_2 R_4) \left(\frac{R_1}{R_2} + i\omega C_1 R_1 + 1 \right) = \left(\frac{1}{R_2} + i\omega C_1 \right) (i\omega C_2 R_3 R_4 + R_3)$

So we get terms linear in ω , quadratic in ω , and constants.

For these to be equal for all ω , we need each of these coefficients to be equal.



(5)

The constant terms are:

$$\left(\frac{R_1}{R_2} + \frac{R_4}{R_3} \right)$$

$$\frac{R_1}{R_2} + 1 = \frac{R_3}{R_2} \Rightarrow \boxed{R_1 + R_2 = R_3}$$

See next page. (11)

The linear terms are: $(1 + \frac{R_1}{R_2}) (C_2 R_3 + C_2 R_4) i\omega + i\omega C_1 R_1 = i\omega (C_2 \frac{R_3 R_4}{R_2} + C_1 R_3)$

$$\Rightarrow C_2 \left(1 + \frac{R_1}{R_2} \right) (R_3 + R_4) + C_1 R_1 = C_1 R_3 + C_2 \frac{R_3 R_4}{R_2}$$

$$\Rightarrow C_2 (R_1 + R_2) (R_3 + R_4) + C_1 R_1 R_2 = (C_1 R_2 + C_2 R_4) R_3$$

~~$$\Rightarrow C_2 R_1 R_3 + C_2 R_1 R_4 + C_2 R_2 R_3 + C_2 R_2 R_4 + C_1 R_1 R_2 = C_1 R_2 R_3 + C_2 R_4 R_3$$~~

~~$$R_3 = R_1 + R_2 \Rightarrow C_2 (R_1 + R_2) (R_1 + R_2) + C_1 R_1 R_2 = C_1 R_2 (R_1 + R_2) + C_2 R_4 (R_1 + R_2)$$~~

$$\Rightarrow C_2 R_3 (R_3 + R_4) + C_1 R_1 R_2 = (C_1 R_2 + C_2 R_4) R_3$$

$$\Rightarrow \boxed{C_2 R_3^2 + C_1 R_1 R_2 = C_1 R_2 R_3} \quad \text{(i)}$$

Equating quadratic terms gives: $(i\omega)^2 (C_2 R_3 + C_2 R_4) C_1 R_1 = (i\omega)^2 C_1 C_2 R_3 R_4$

$$\Rightarrow C_1 C_2 R_1 R_3 + C_1 C_2 R_1 R_4 = C_1 C_2 R_3 R_4$$

$$\Rightarrow R_1 (R_3 + R_4) = R_3 R_4$$

$$R_3 = R_1 + R_2 \Rightarrow R_1 (R_1 + R_2) = R_4 ((R_1 + R_2) - R_1)$$

$$\Rightarrow \boxed{R_4 = \frac{R_1 (R_1 + R_2)}{R_2}} \quad \text{(11)} \quad \text{(11)}$$

$$\text{Also, (i)} \Rightarrow C_2 = C_1 R_2 \frac{(R_3 - R_1)}{R_3^2} = C_1 R_2 \frac{(R_1 + R_2 - R_1)}{(R_1 + R_2)^2} = \frac{R_2^2}{(R_1 + R_2)^2} C_1 \Rightarrow \boxed{C_2 = \frac{R_2^2}{(R_1 + R_2)^2} C_1}$$




(6)

Note that $\textcircled{11}$ and $\textcircled{11} \textcircled{11}$ can be obtained directly by

taking the $\omega \rightarrow 0$ limit (for $\textcircled{11}$), where the capacitors don't (i.e., DC)

let any current through so that we have

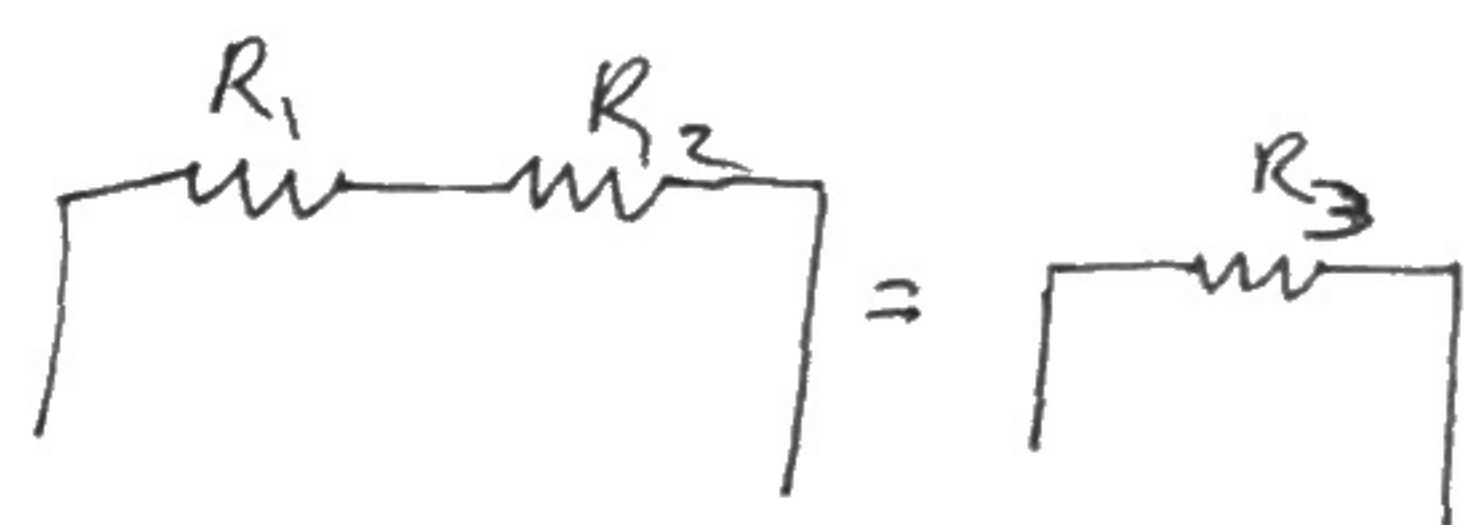

and $\omega \rightarrow \infty$ where the impedance of C_1, C_2 vanishes so that

we have

